

ELEC 4700 Assignment 4
Circuit Modeling
April 7, 2019
Chad Blanchette 100968854

Part 1:

The code from this part was pulled from my PA 9 work which formulated the MNA equations to solve the nodal voltages and currents. The following 4 figures are plots from PA 9.

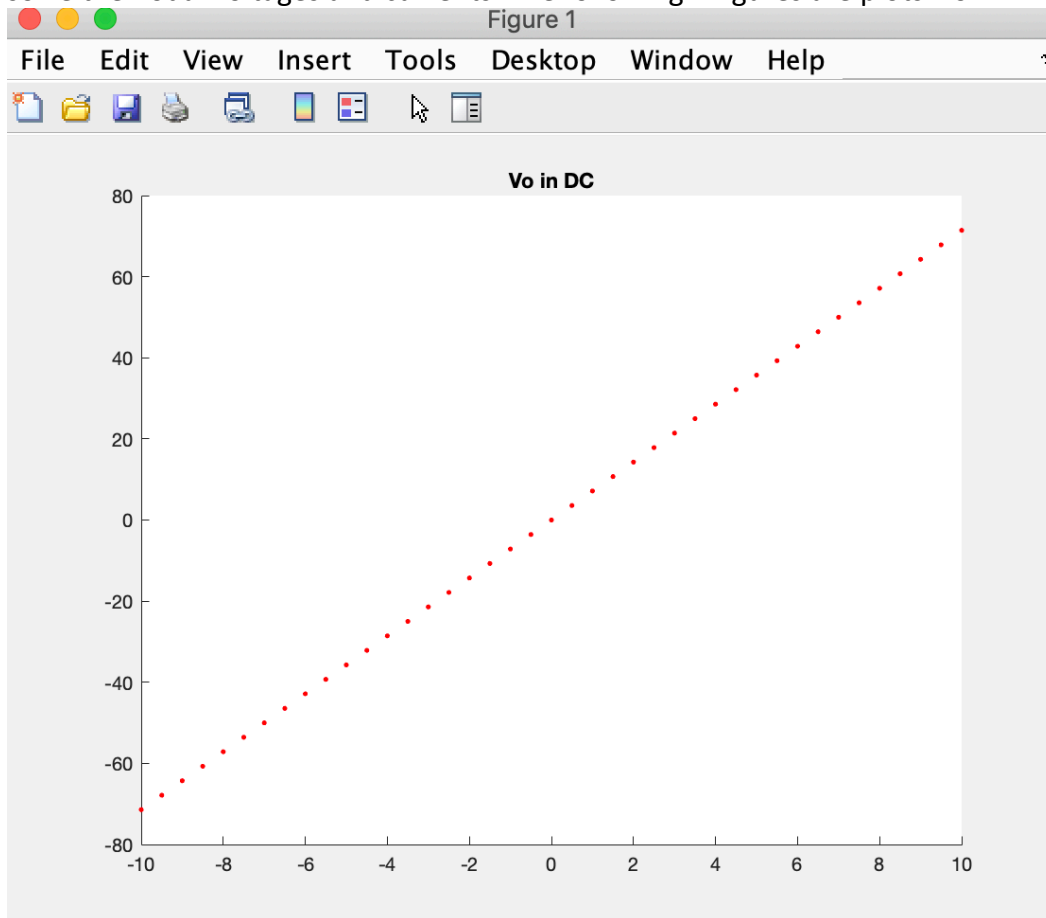


Figure 1: Voltage Output in DC

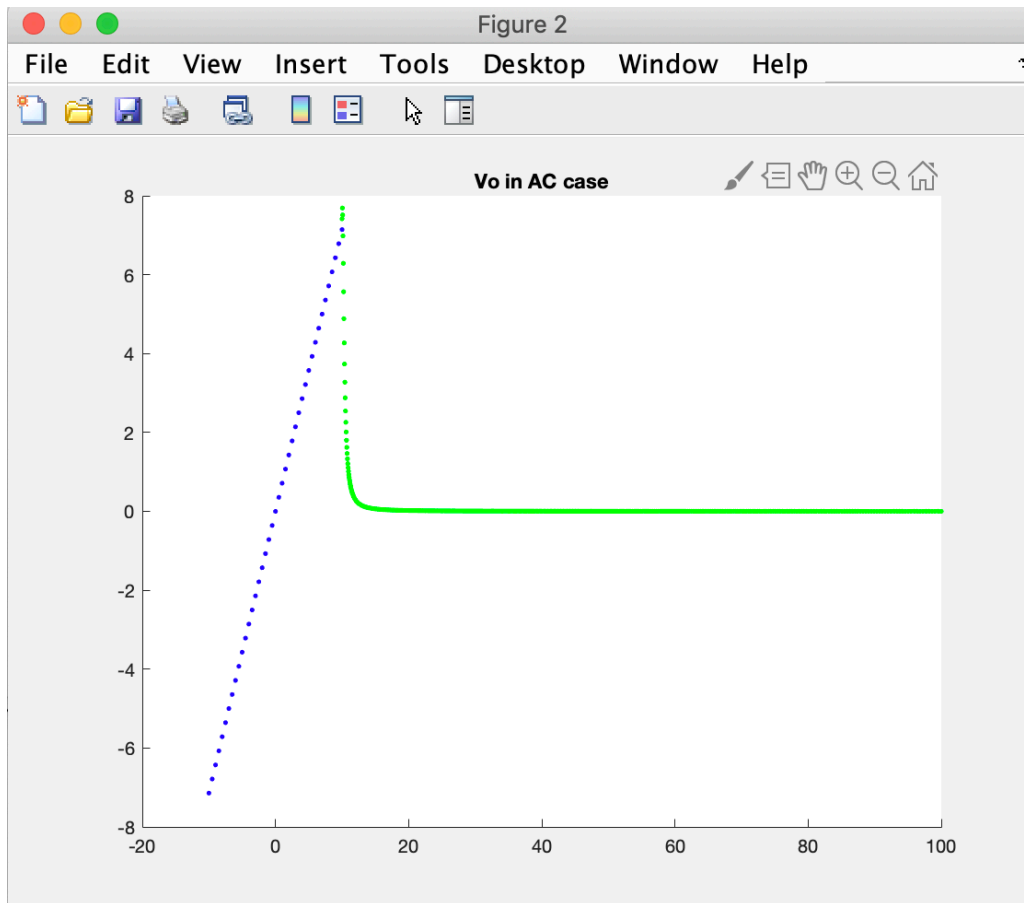


Figure 2: Output Voltage in AC

```

-      G= [G1 0 0 0 0 0 0;
          -G1 G1+G2 -1 0 0 0 0;
           0 1 0 -1 0 0 0;
           0 0 -1 G3 0 0 0;
           0 0 0 0 -a 1 0;
           0 0 0 G3 -1 0 0;
           0 0 0 0 0 -G4 G4+Go];
-      C= [0 0 0 0 0 0 0;
          -c c 0 0 0 0 0;
           0 0 -L 0 0 0 0;
           0 0 0 0 0 0 0;
           0 0 0 0 0 0 0;
           0 0 0 0 0 0 0;
           0 0 0 0 0 0 0];

```

G and C matrices

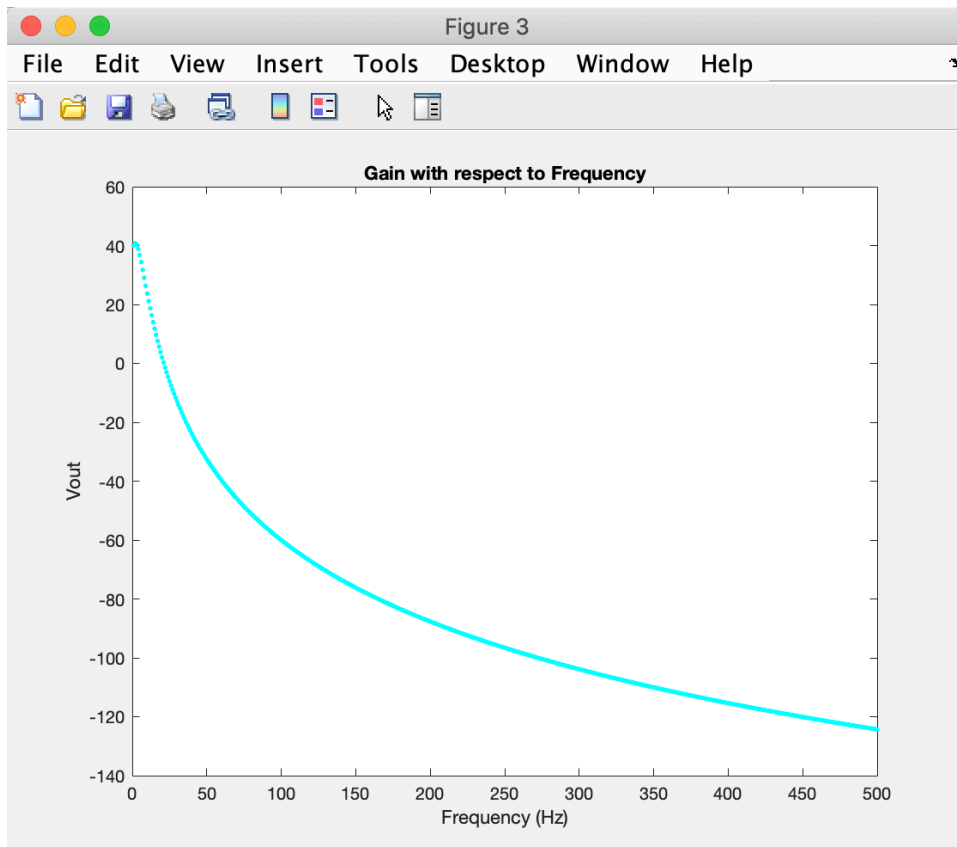


Figure 3: Voltage Gain compared to Frequency

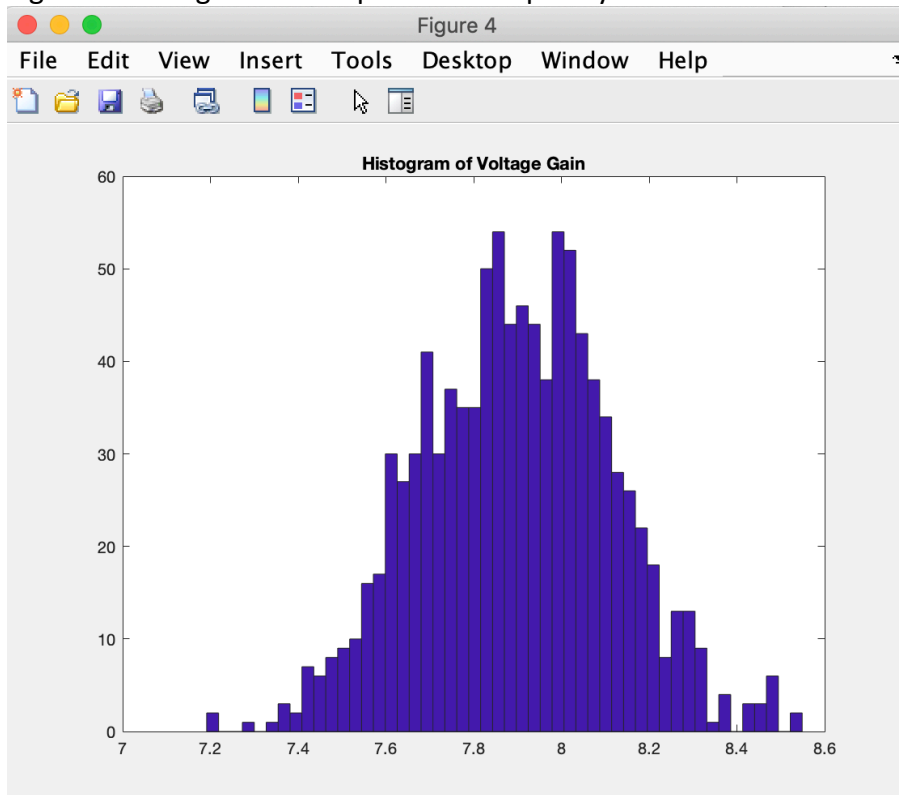


Figure 4: Histogram of Voltage Gain

Part 2:

The following figures will show the effects of a transient system compared to the original.

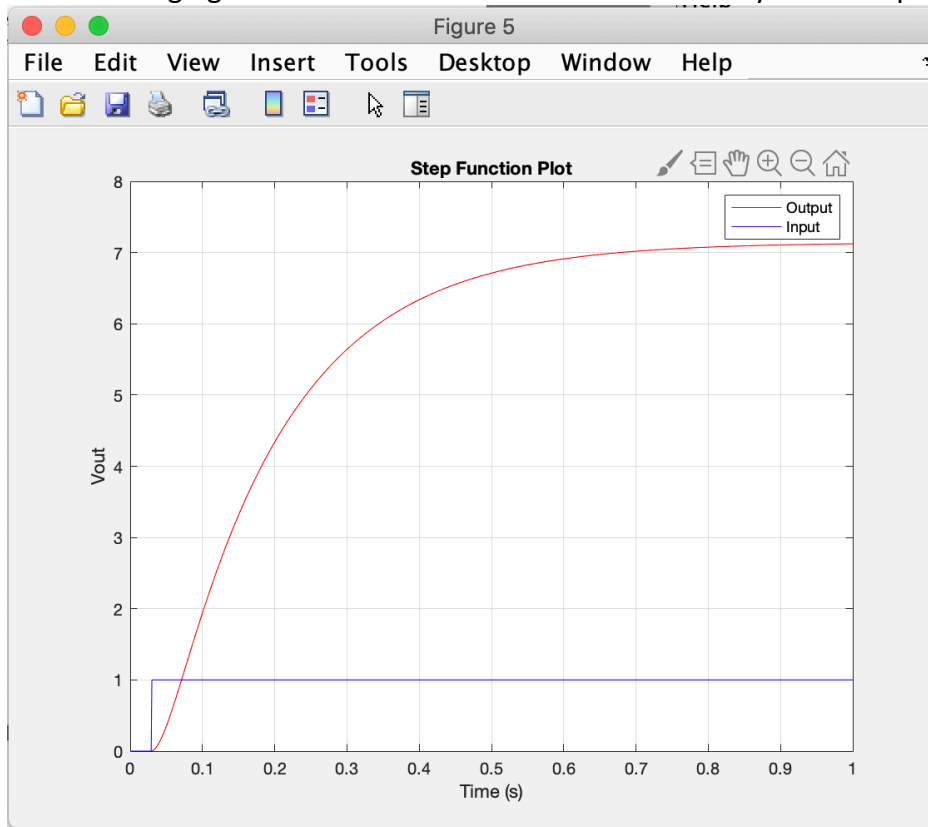


Figure 5: DC input and AC output

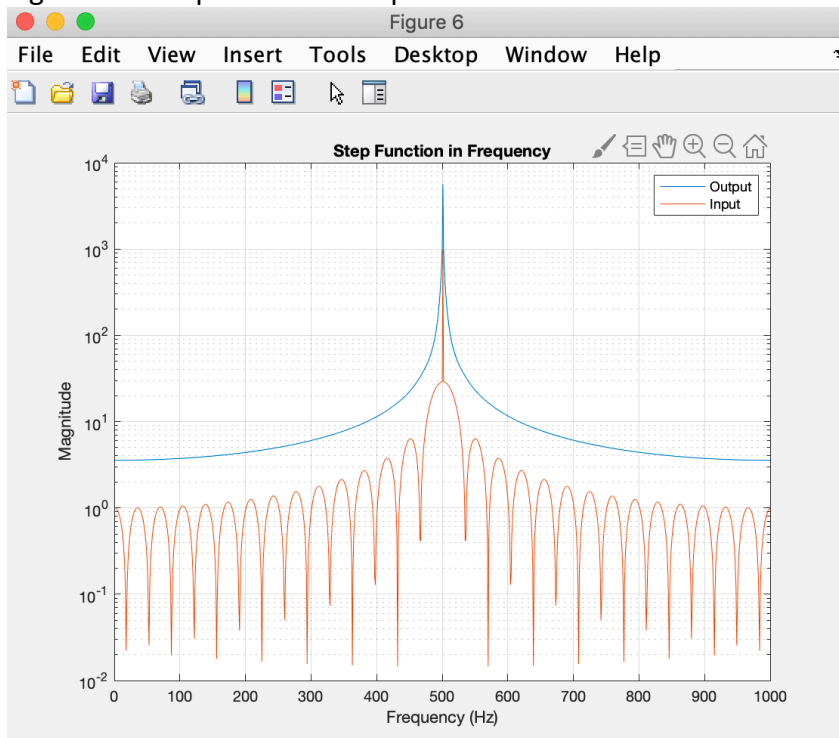


Figure 6: Vin and Vout with respect to Frequency

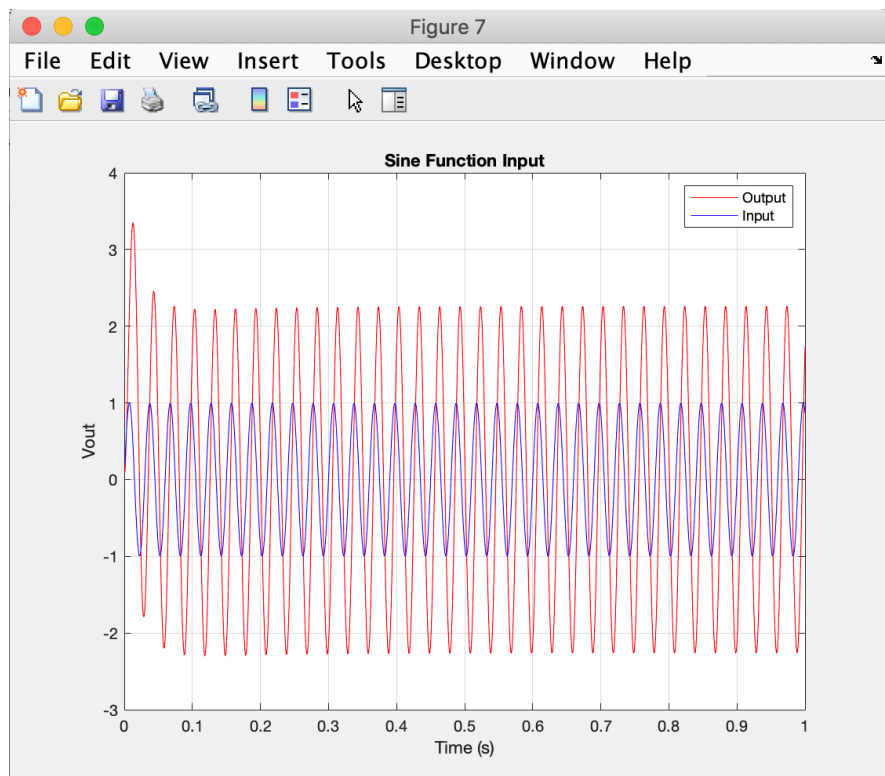


Figure 7: Sine function from part 2d

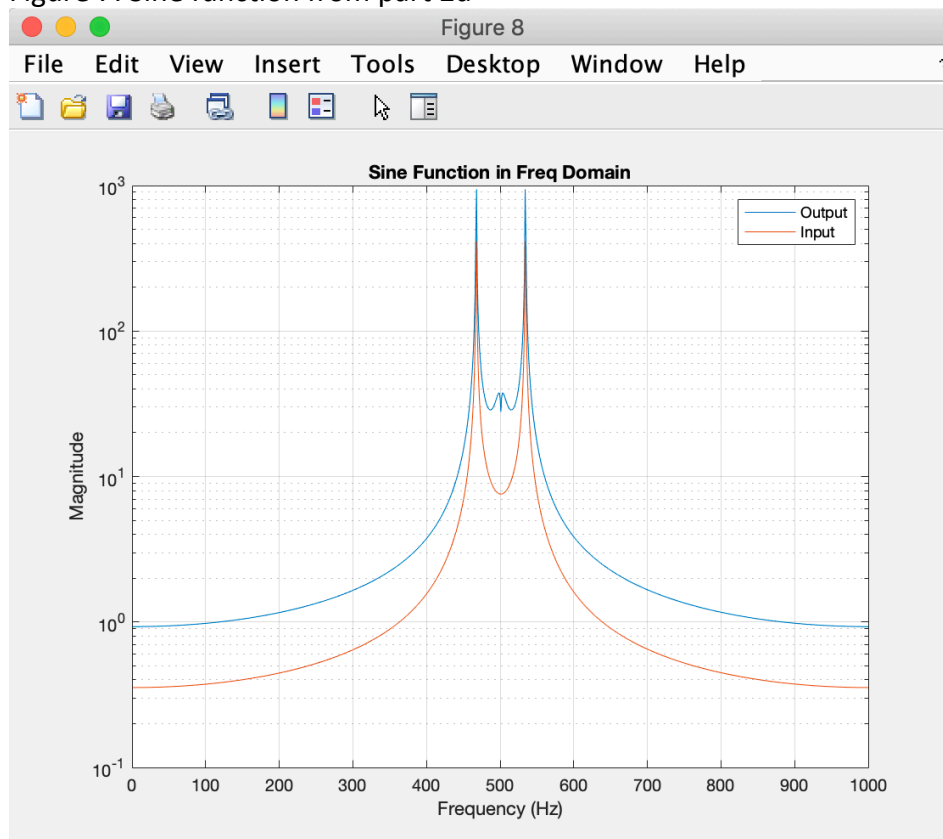


Figure 8: Sine function at different frequencies

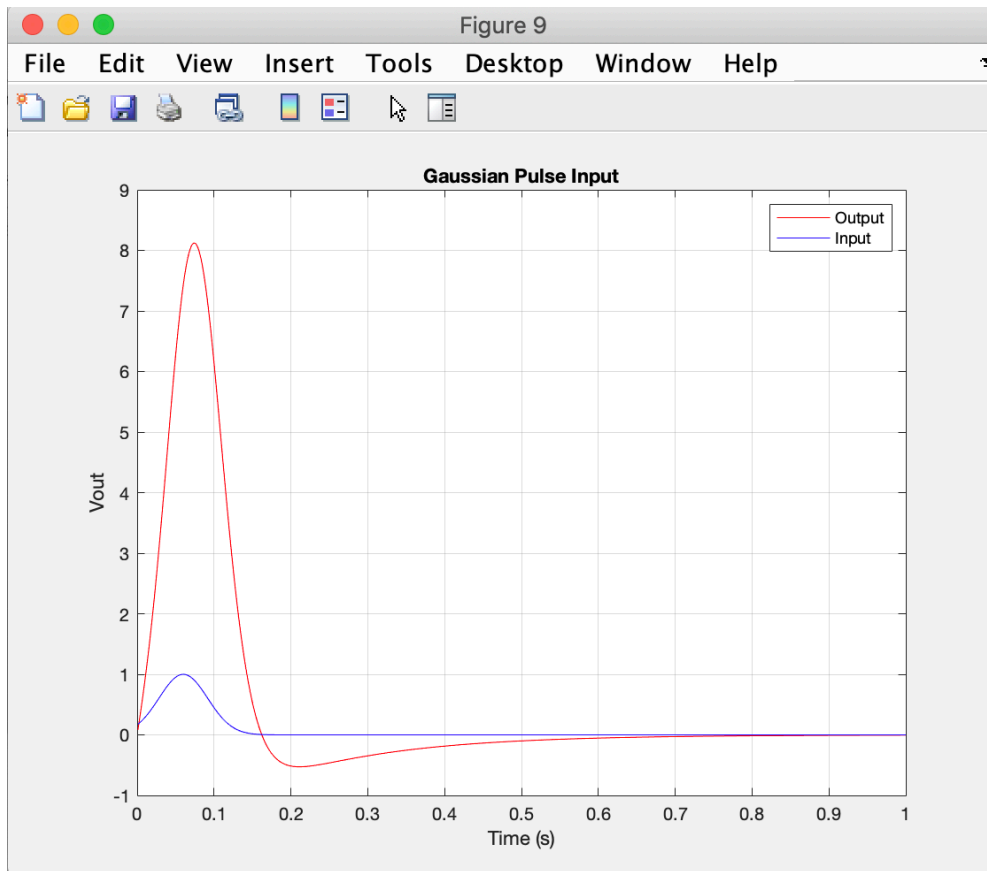


Figure 9: Part 2C Vin and Vout in time domain

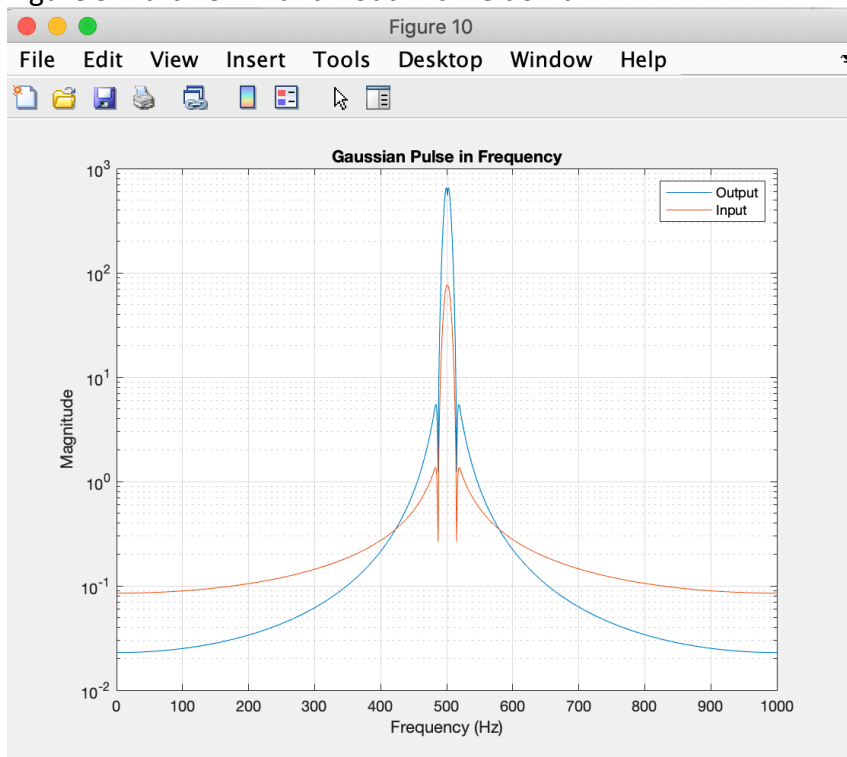


Figure 10: Fourier Transform of Frequency Response

Part 3

The following figures will show how noise affects the circuit simulations.

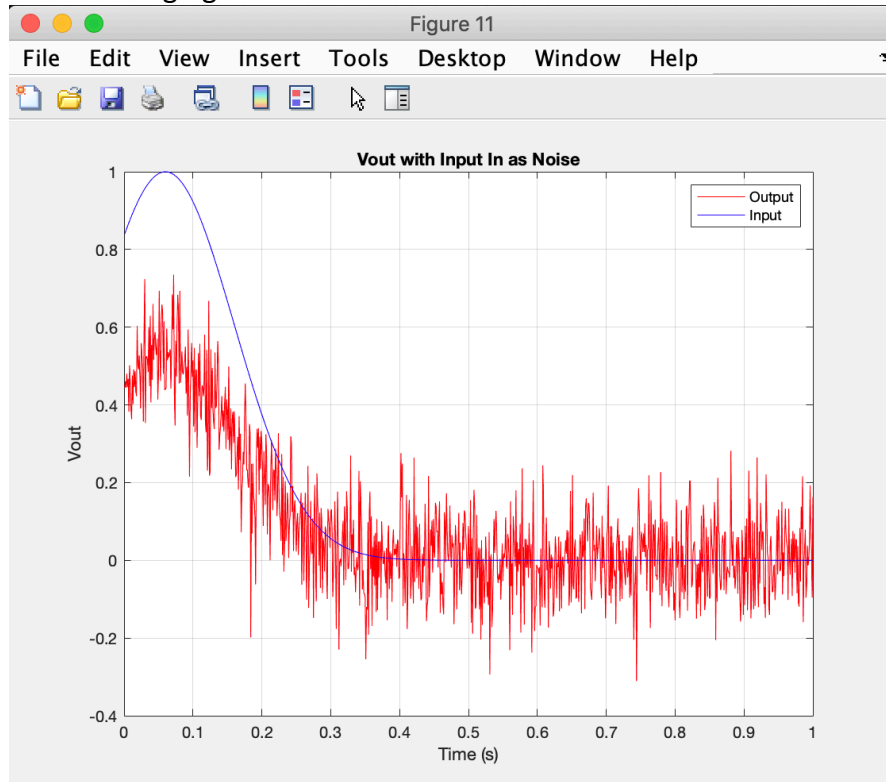


Figure 11: Vout and Vin with noise added to the circuit with time

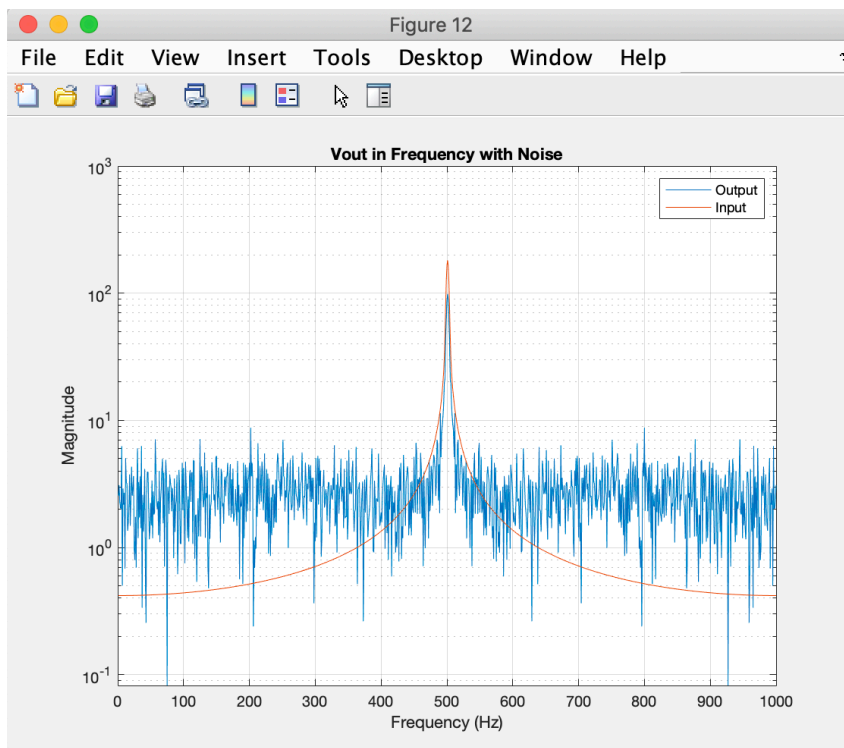


Figure 12: Vout and Vin with noise added to the circuit with frequency